

## LAB-4

*Due to:*

*Part 1: Sunday, April 24, 2016, 23:55hrs*

*Submission: via COW*

### Part 1: ISBN\_Memory (Individual Work)

(This part of the lab will be performed and submitted individually.)


#### Problem Definition

In this part of your assignment you are going to implement a specific kind of memory called ISBN\_RAM as a verilog module.

There are two modes in this ISBN\_RAM, write and read. In the write mode, the module takes a 12-bit binary number with **data** and **check** bits as input. Then it controls the **data** and **check** bits and writes 9 **data** bits to the memory.

In the read mode, the module reads 9-bit **data** from RAM, adds 3 **check** bits and produces 12 bit output that contains both **data** and **check** bits.

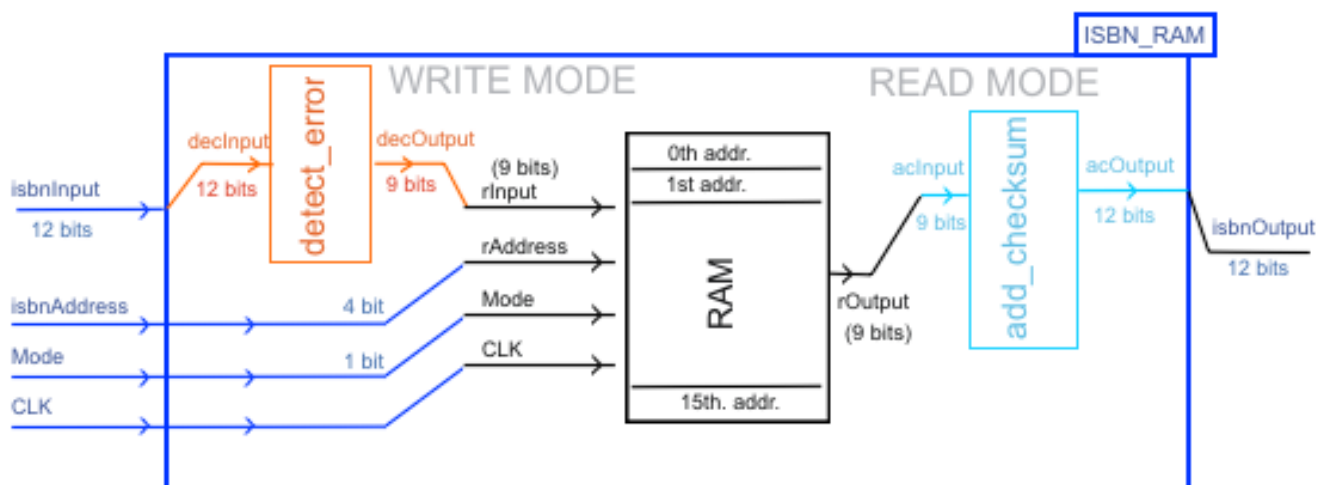The module structure is given in the figure below:



## Add\_checksum Module:

Add\_checksum module takes a 9 bit binary number(**acInput**) that consist of only **data** bits. For error checking, it adds 3 **checksum** bits and gives 12 bit output.

Input( <b>acInput</b> ) Format									
Bit position	1	2	3	4	5	6	7	8	9
	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$

Above,  $d_1$  is the most significant bit and  $d_9$  is the least significant bit.

- Checksum is a 3-bit binary number ( $c_1c_2c_3$ ) where  $c_1$  is the most significant bit and  $c_3$  is the least significant bit. The checksum is calculated using the following formula;

$$checksum = \left( \sum_{i=1}^9 i * d_i \right) \text{ modulus } 8$$

*Equation 1*

- Output (**acOutput**) consists of 9 data and 3 checksum bits. 3 checksum bits  $c_1$ ,  $c_2$  and  $c_3$  must be located at positions 10, 11 and 12 respectively. Also data bits  $d_1$  to  $d_9$  must be located at positions 1, 2, ..., 9 respectively.

Output( <b>acOutput</b> ) Format												
Bit position	1	2	3	4	5	6	7	8	9	10	11	12
	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	$c_1$	$c_2$	$c_3$

- Use the following Verilog definition for the module:

```
module add_checksum(  
    input [1:9] acInput,  
    output reg [1:12] acOutput  
);
```

- Sample input and outputs are given below;

INPUT										OUTPUT											
$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$		$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	$c_1$	$c_2$	$c_3$
1	0	1	0	1	0	1	0	1		1	0	1	0	1	0	1	0	1	0	0	1
1	1	1	1	1	1	1	1	1		1	1	1	1	1	1	1	1	1	1	0	1

### Detect\_error Module:

Detect\_error module takes a 12 bit binary number (**decInput**) that consist of both **checksum** and **data** bits. It calculates checksum ( $c_1'c_2'c_3'$ ) of 9 **data** bits and compares it with 3-bit checksum part ( $c_1c_2c_3$ ) of the decInput. If they are equal then gives the **data** bits ( $d_1 \dots d_9$ ) as output, otherwise gives 000000000 as output.

Input( <b>decInput</b> ) Format												
Bit position	1	2	3	4	5	6	7	8	9	10	11	12
	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	$c_1$	$c_2$	$c_3$

- 3 checksum bits  $c_1$ ,  $c_2$  and  $c_3$  are located at positions 10,11 and 12 respectively.
- The rest are the 9 data bits where  $d_1$  is the most significant bit and  $d_9$  is the least significant bit.
- You can assume that 9 data bits will not be equal to all zeros.
- The checksum ( $c_1'c_2'c_3'$ ) of 9 input data bits is calculated according to the Equation 1.
- If the calculated checksum ( $c_1'c_2'c_3'$ ) equals to the given checksum ( $c_1c_2c_3$ ) then 9 data bits ( $d_1 \dots d_9$ ) are given as output.
- If the calculated checksum ( $c_1'c_2'c_3'$ ) does **not** equal to the given checksum ( $c_1c_2c_3$ ) then 000000000 (9 zero bits) is given as output.

Output( <b>decOutput</b> ) Format									
Bit position	1	2	3	4	5	6	7	8	9
	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$

- Use the following Verilog definition for the module:


```
module detect_error(
    input [1:12] decInput,
    output reg [1:9] decOutput
);
```

- Sample input and outputs are given below;

INPUT												OUTPUT									
$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	$c_1$	$c_2$	$c_3$	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	
1	0	1	0	1	0	1	0	1	0	0	1	1	0	1	0	1	0	1	0	1	
1	0	1	0	1	0	1	0	1	0	1	1	0	0	0	0	0	0	0	0	0	
 
## RAM Module

The RAM will use 4-bit addresses. Each address will contain 9 bits of data, i.e. a memory *word* consists of 9 bits. Design the following RAM in verilog:



- Initially all RAM contains 9'b111111111 values.
- Mode(1 bit):
  - 0 - read mode:** Data stored at **rAddress** location of the RAM must be represented in **rOutput** when the positive edge **CLK** pulse comes.
  - 1 - write mode:** **rInput** must be stored at **rAddress** location of the RAM when the

positive edge **CLK** pulse comes.

- Use the following lines as the port definition of the **RAM**:

```
module RAM(
    input [8:0] rInput,
    input CLK,
    input Mode, //0:read, 1:write
    input [3:0] rAddress,
    output reg [8:0] rOutput
);
```

## ISBN\_RAM Module:

Three modules (RAM, detect\_error and add\_checksum) described above will be used by an upper module in which inputs and outputs of the other modules are defined. **You should not edit this module.**

- The module definition for the main module is below:

```

module ISBN_RAM(
    input [11:0] isbnInput,
    input CLK,
    input Mode, //0:read, 1:write
    input [3:0] isbnAddress,
    output [11:0] isbnOutput
);

```

- Sample write and read operations are given below;

isbnAddress	Mode	isbnInput (red bits are erroneous bits)													isbnOutput
		$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$d_8$	$d_9$	$c_1$	$c_2$	$c_3$		
0000	1(write)	1	0	1	0	1	0	1	0	1	0	0	1	will not be checked	
0001		1	0	1	0	1	0	1	0	1	0	1	1	will not be checked	

[illegible]

## Hints

- You should not edit ISBN\_RAM Module. It will be provided for you and will not be implemented by you.
- “RAM”, “detect\_error”, “add\_checksum” and “ISBN\_RAM” modules will be tested **separately**.

## Deliverables:

- Implement both modules in a single Verilog file: lab4\_1.v. Do NOT submit your testbenches, or project file (.xise).
- You can share your testbenches on the newsgroup.
- Submit the file through the COW system before the given deadline.
- This part is required to be done individually, not with your partner. Any kind of cheating is not allowed.
- Use the newsgroup metu.ceng.course.232 for any questions regarding to the homework.